AEP227 Github Name

November 27, 2019

ECE 4540: VLSI Circuit Design


Lab 4 Report

Contents


Part I: Pre-Layout Design	2
Schematics of 4-bit Ripple Carry Adder and Sub-Components	
Test Bench, Pre-Layout Simulation	
Part II: Layout, Post-Layout Simulations, Adder Characteristics	
Adder Layout	
Post-Layout Simulation, Worst-Case Propagation Delay	
Part III: Bonus 4-bit PG Ripple Carry Adder	8
Schematic of 4-bit Ripple Carry Adder	8
Test bench and Pre-Layout Simulation	

Part I: Pre-Layout Design

 
Schematics of 4-bit Ripple Carry Adder and Sub-Components




1-bit Full Adder Schematic

 


4-bit Ripple Carry Adder Schematic

 


 4-bit Ripple Carry Adder Testbench Schematic



 Simple addition case to test functionality of the circuit and determine pre-layout worst-case delay Initially, A = 1111, B = 0000, and the carry-in was 0. This resulted in the correct output of 01111 At 10ns, B was changed to 0001, resulting in the correct output of 10000



 


B0 changed to 1 at 10.1252ns. The carryout of the 4-bit adder updated to 1 at 10.35ns Worst-case propagation time = 0.2248ns


Part II: Layout, Post-Layout Simulations, Adder Characteristics

Adder Layout




 


4-bit Ripple Carry Adder DRC Pass

 

4-bit Ripple Carry Adder LVS Pass

 


4-bit Ripple Carry Adder PEX Pass

 


Part III: Bonus 4-bit PG Ripple Carry Adder


Schematic of 4-bit Ripple Carry Adder

 


 
Schematic of the 4-bit PG Ripple Carry Adder



 Testbench for 4-bit PG Ripple Carry Adder



 

 

B_0 switched to 1 at 10.1228ns, output S_2 updated at 10.3007ns.

"Average" propagation delay: 0.1779ns